



# SPIICE for the Complete Idiot

---

C. H. Ting  
Silicon Valley FIG  
4/30/2005



# TRANSISTORS AND DIODES

---

- Junction Diodes
- Diode Model (D)
- Bipolar Junction Transistors (BJTs)
- BJT Models (NPN/PNP)
- Junction Field-Effect Transistors (JFETs)
- JFET Models (NJF/PJF)
- MOSFETs
- MOSFET Models (NMOS/PMOS)
- MESFETs
- MESFET Models (NMF/PMF)



# TYPES OF ANALYSIS

---

- DC Analysis
- AC Small-Signal Analysis
- Transient Analysis
- Pole-Zero Analysis
- Small-Signal Distortion Analysis
- Sensitivity Analysis
- Noise Analysis



# Device Models

---

- R Semiconductor resistor model
- C Semiconductor capacitor model
- SW Voltage controlled switch
- D Diode model
- NPN NPN BJT model
- PNP PNP BJT model
- NMOS N-channel MOSFET model
- PMOS P-channel MOSFET model



# SUBCIRCUITS

---

- .SUBCKT Line
- Subcircuit Calls
- Subcircuit Calls
- ...
- .ENDS Line



# VOLTAGE AND CURRENT SOURCES

---

- Independent Sources
  - Pulse
  - Sinusoidal
- Linear Dependent Sources
  - Linear Voltage-Controlled Current Sources
  - Linear Voltage-Controlled Voltage Sources
  - Linear Current-Controlled Current Sources
  - Linear Current-Controlled Voltage Sources
- Non-linear Dependent Sources



# Spice for Logic Simulation

---

\* Simulation of NAND gate

```
.control
```

```
destroy all
```

```
run
```

```
plot out1+30 out+24 set+18 clr+12 in1+6 in2
```

```
.endc
```

```
.tran 60p 100n 10p UIC
```

```
*x13 in1 in2 out NAND
```

```
.subckt NAND in1 in2 out
```

```
e1 out 0 value=if((v(in1)>2.5 && v(in2)>2.5), 0, 5)
```

```
.ends
```

```
end
```



# Spice for Logic Simulation

---

- NAND
- NOR
- XOR
- INV
- TG
- DFF





# Spice for Analog Circuits

---

- OpAmp

```
.subckt OPAMP in1 in2 out  
e1 out 0 in1 in2 100000  
.ends
```

- Comparator

```
.subckt COMPARE in1 in2 out  
e1 out 0 value=if((v(in1)>v(in2)), 5, 0)  
.ends
```



# Spice for Analog Circuits

---

- Integrator

```
.subckt INTEGRATE in1 in2 out control  
x1 in1 in out OPAMP  
r1 in2 in 1k  
r2 out in r=v(control)>1 ? 1meg : 50  
c1 out in 5p  
.ends
```



# Spice for DSO Timebase

---


- Triggering unit
- Timebase unit


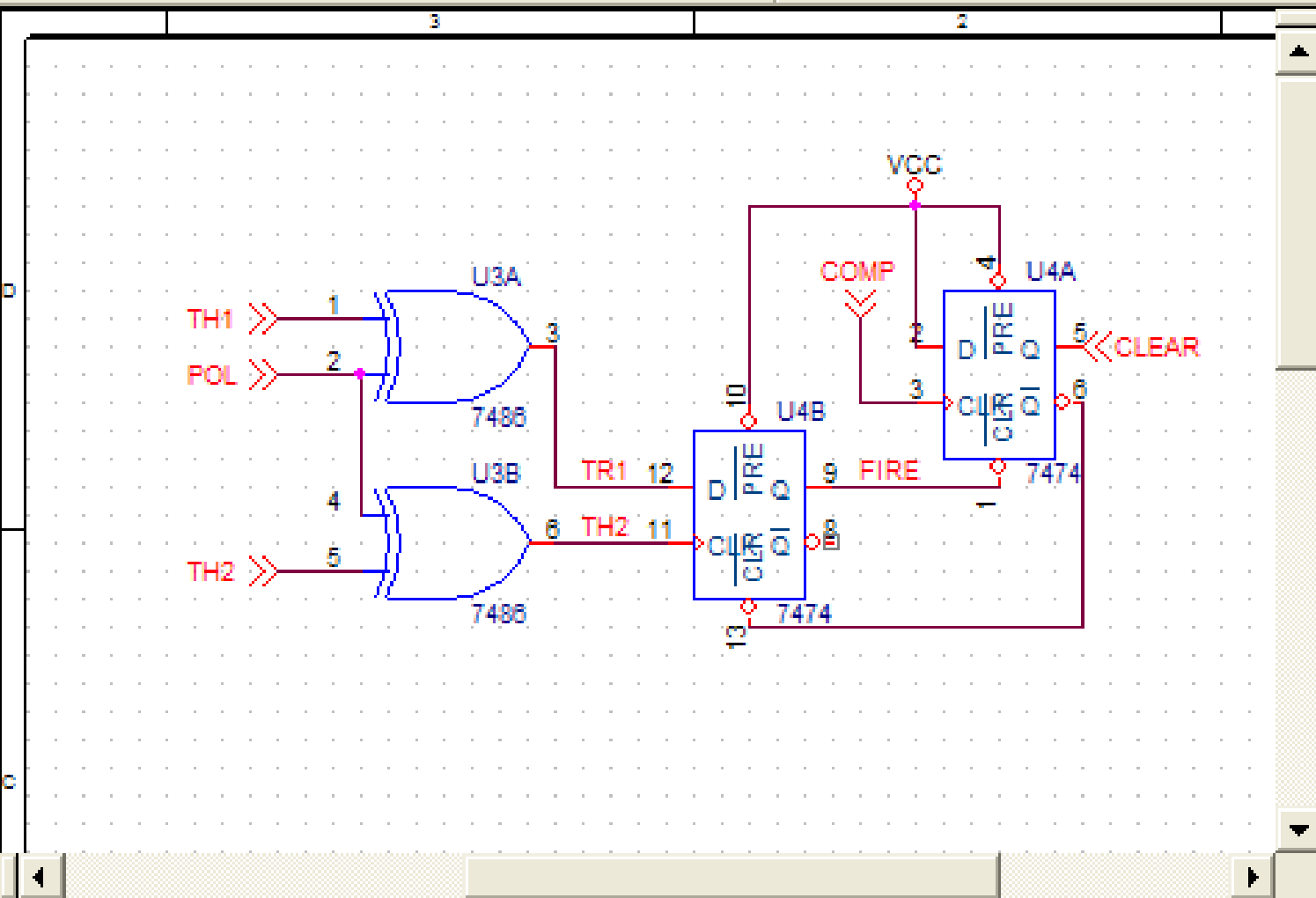
# Spice of DSO Core Circuit

---

- Trigger Unit
  - 2 XOR
- Timebase Unit
  - 2 DFF for firing and clearing
- Schematics
- Spice source code
- Simulation wave forms



Navigation and tool icons for the OrCAD Capture interface, including a mouse cursor, eraser, and various selection tools.



# Spice of DSO Timebase

---


- Schematics
- Spice source code
- Simulation wave forms


 
# Concluding Remarks

---

- WinSpice is very useful in logic simulation
- A simple template is very easy to adapt to many applications
- It allow us to consider building mixed signal ASIC chips



Thank you